




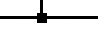

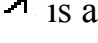
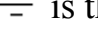
How to Read a Schematic And Basic Electronics Test Answers


Table Of Contents

[Previous: Reading A Schematic & Basic Electronics](#)

[Next: Programming Part 1](#)

Page 11:

- 1) B) Schematic
- 2) D) Switch
- 3) A) Resistor
- 4) E) Ohm, B) Ohm's Law
- 5) A) Amperes (or Amps), E) Milliamps (or Ma or ma)
- 6) C) Capacitors
- 7) B) Diode
- 8) D) Integrated Circuits
- 9) B) Operational Amplifier
- 10) This  shows unconnected conductors.
- 11) This  is a resistor.
- 12) This  is a switch.
- 13) This  is connected conductors.
- 14) This  is a capacitor.
- 15) This  is a diode.
- 16) This  is the symbol for ground.
- 17) Ohm's Law: $V = IR$
- 18) $I = 4$, $R = 10$ so $V = IR = 40$ Volts
- 19) $V = 12$, $R = 6$ so $I = V/R = 2$ Amps
- 20) $I = 75$, $V = 150K$ Volts so $R = V/I = 150K/75 = 2K$ Ohms
- 21) $P = VI = 150K * 75 = 11,250,000$ Watts
- 22) 25K ohms

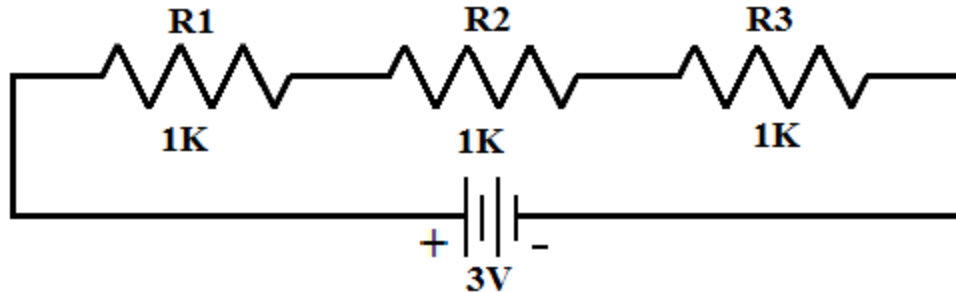Page 13:

So, the total resistance in the above circuit = 3000 ohms

Now, remember that the current in a circuit = $I = V/R$.

The voltage is 3 volts

So, remembering to write the equation first, plug in the values to get the current:

$$I = \frac{V}{R} = \frac{3}{3000} = \underline{1} \text{ ma}$$

Since all three resistors are 1000 ohms in the above circuit, there is a total of 3000 ohms, and $I = 3/3000 = 1\text{ma}$. Remember, ma means milliamps or thousandths of an amp, so 1ma is the same as $1/1000^{\text{th}}$ of an amp. Now, to find the voltage across each 1K resistor, use $V = IR$.

So, the **calculated** voltage across each resistor =

$$V = IR = \underline{1\text{ma}} * \underline{1000} = \underline{1 \text{ volt}}$$

Page 16:

Would including a 10K resistor work? No, because that would make the whole circuit more than 10K ohms.

Page 19:

$1,385,247^0 = \underline{1}$ (**anything** raised to the power of 0 is 1)

$1 \times 10^3 = \underline{1000}$ (any time you have 1×10 raised to a power, just write down 1, then the number of zeros indicated by the exponent – 3 in this case)

$.1\text{ma} = \underline{1/10000}$ amps (remember that ma means milliamps, and that mili means $1/1000^{\text{th}}$. This is $1/10^{\text{th}}$ of that, which is $1/10000$)

$10^1 = \underline{10}$ (anything raised to the power of 1 is itself)

$10^{-4} = \underline{.0001}$ or $\underline{1/10000}$ (remember to start with a 1 followed by a decimal, then move the decimal to the left the number of places shown by the negative exponent)

For the number 432.178,

the 4 is in the 100 s place,

the 7 is in the 1/100 s place, and

the 8 is in the 1/1000 s place.

x raised to the power of y which is raised to the power of 0 = x

Break it down: y raised to the power of 0 is 1, then x raised to the power of 1 is x .

Page 22:

But since you know the voltage, you can use the rules for a parallel circuit and Ohm's law for resistance and current. So calculate the following. Remember, the voltage is 3 volts across each resistor. Also remember to write Ohm's law for current first, which is $I = V/R$:

Current through R1: $I = V/R = 3/30K = .1 \text{ ma}$ (.0001 amp)

Current through R2: $I = V/R = 3/300 = .01 \text{ amp}$

Current through R3: $I = V/R = 3/3K = 1 \text{ ma}$ (.001 amp)

Total current through all 3 = 11.1 ma (.0111 amp)

Since you know the source voltage is 3 volts and you know the total current, you can calculate the combined resistance using Ohm's law for resistance, which is $R = V/I$:

$R_{\text{Total}} = \underline{R = V/I} = 3/.0111 = 270 \text{ ohms}$